

Excitation Table for SR flip flop.

Truth table.

S	R	P.S Q_n	N.S Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Undefined
1	1	1	

Excitation table.

P.S Q_n	N.S Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$(00) \begin{pmatrix} 0 & 0 \\ 0 & 1 \end{pmatrix} \} 0 \times$
 $(01) \begin{pmatrix} 0 & 0 \\ 0 & 1 \end{pmatrix}$
 $(10) \begin{pmatrix} 0 & 0 \\ 0 & 1 \end{pmatrix}$
 $(11) \begin{pmatrix} 0 & 0 \\ 1 & 0 \end{pmatrix} \} X 0$

Excitation table for D flip flop.

Truth table.

D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Excitation table.

Q_n	Q_{n+1}	D
0	0	0
0	1	0
1	0	1
1	1	1

0 0 \rightarrow 0

0 1 \rightarrow 1

1 0 \rightarrow 0

1 1 \rightarrow 1

Excitation Table of JK flip flop.

Truth table.

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation table.

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

$(00) \begin{pmatrix} 0 & 0 \\ 0 & 1 \end{pmatrix} \} 0x$
 $(10) \begin{pmatrix} 0 & 1 \\ 1 & 1 \end{pmatrix} \} x1$
 $(01) \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix} \} 1x$
 $(11) \begin{pmatrix} 0 & 0 \\ 1 & 0 \end{pmatrix} \} x0$

Excitation table for T flip flop.

Truth table.

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table.

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

$00 \rightarrow 0$

$01 \rightarrow 1$

$10 \rightarrow 1$

$11 \rightarrow 0$

Flip flop Conversion

Steps:

- Consider truth table for destination flip flop & extend it as excitation table of source flip flop.

- Draw K-map for source flip flop output variables, it will provide expression for conversion.

- Draw the circuit according to K-map expression.

Conversions: $SR \rightarrow D$ $JK \rightarrow T$ $T \rightarrow D$
 $SR \rightarrow JK$ $JK \rightarrow D$ $D \rightarrow T$
 $SR \rightarrow T$

S-R to D flip flop Conversion

Truth table of D (i)

D	Q_n	Q_{n+1}
0	x	0
1	x	1

Excitation table for SR.


Q_n	Q_{n+1}	SR
0	0	0x
0	1	10
1	0	01
1	1	x0

Truth table

excitation table
S SR


D	Q_n	Q_{n+1}	S	R
0	0	0	0	x
0	1	0	0	1
1	0	1	1	0
1	1	1	x	0

(ii) K-map for S

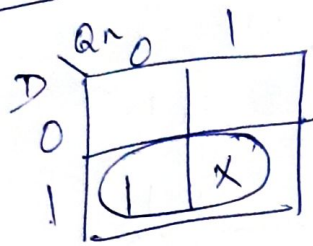


$$S = D$$

K-map for R.

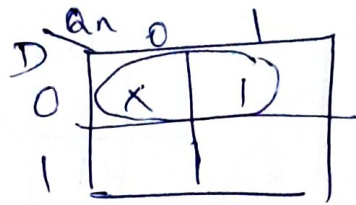

$$R = \bar{D}$$

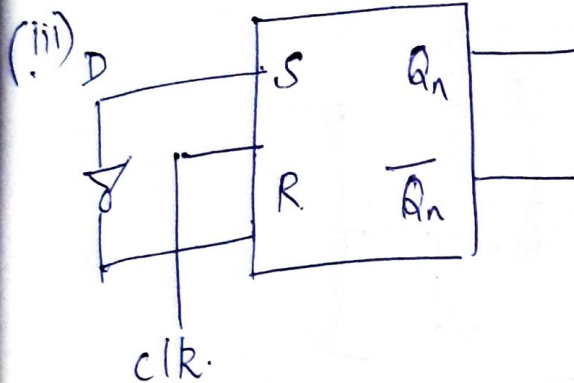

S-R to J-K flip flop conversion

Truth table of J-K.

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

Truth table of JK.

Excitation table of SR.

(i)

J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

E.T of SR.

Q_n	Q_{n+1}	SR
0	0	0X
0	1	10
1	0	01
1	1	X0

ii) K-map for S


J \ K Q _n	00	01	11	10
0		X		
1	1	X		1

$$S = \overline{J} \overline{K} \overline{Q}_n$$

Kmap for R

J \ K Q _n	00	01	11	10
0	X	X	1	X
1			1	

$$R = K Q_n$$

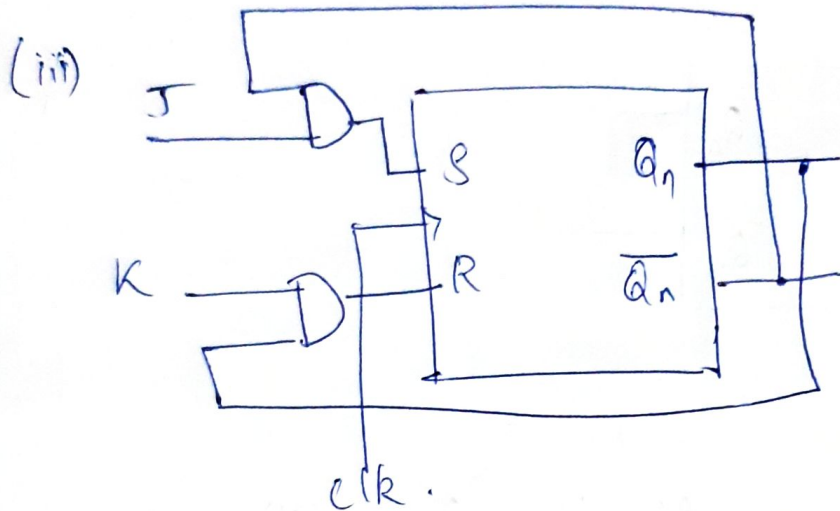


SR flip flop to T flip flop Conversion

T	T	T.F.F.
T	Q _n	Q _{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

E.T	S	R	F.F.
Q _n	Q _{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


T	T	T	F.T	S	R
T	Q _n	Q _{n+1}	S	R	
0	0	0	0	X	
0	1	1	X	0	
1	0	1	1	0	
1	1	0	0	1	

ii) K-map of S

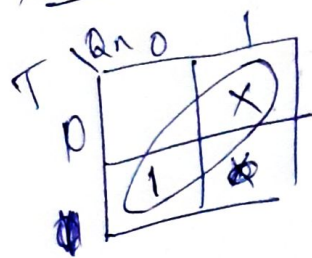


$$S = T \oplus Q_n$$

K-map of R.

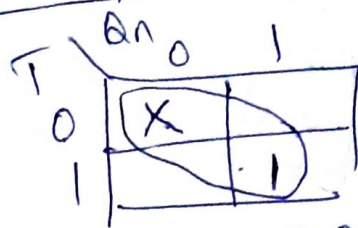

$$R = T \oplus Q_n$$

iii)

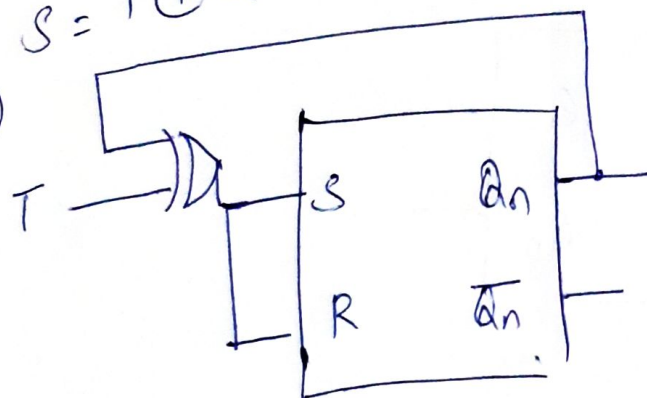

J-K to T flip flop conversion

T.T & T.F.F

T	Qn	Qn+1
0	0	0
0	1	1
1	0	1
1	1	0

E.T & J.K.F.F.

Qn	Qn+1	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

ii)

T	Qn	Qn+1	J	K
0	0	0	0	X
0	1	1	X	0
1	0	1	1	X
1	1	0	X	1

(ii*) K-map for J

Q_n	0	1
0		X
1	1	X


$$J = T$$

K-map for K

Q_n	0	1
0	X	
1	X	1

$$K = T$$

(iii)

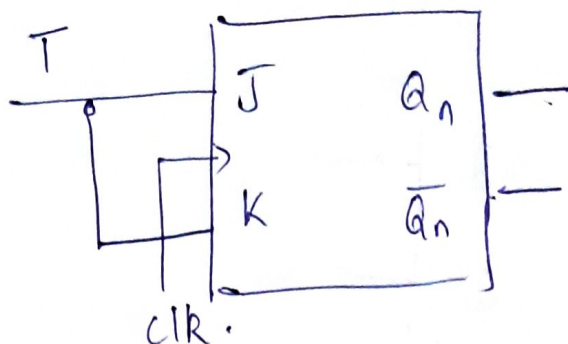

J-K to D flip flop conversion

T.T & D.F.F

T	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

E.T & J.K.

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

i)

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	X	1
1	0	1	X
1	1	X	0

ii) K-map for J

Q_n	0	1
0		X
1	1	X


$$J = D$$

K-map for K

Q_n	0	1
0	X	1
1	X	

$$K = \overline{D}$$

iii)

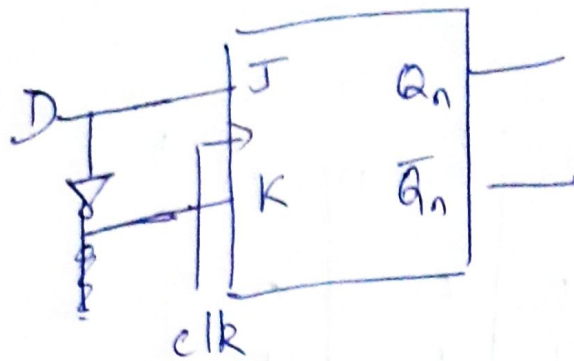

T to D flip flop conversion

T.T & D.F.F. T.T & D.F.F. E.T & T.F.F.

D	Qn	Qn+1
0	0	0
0	1	0
1	0	1
1	1	1


(i)

D	Qn	Qn+1	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

E.T & T.F.F.


Qn	Qn+1	T
0	0	0
0	1	1
1	0	1
1	1	0

(ii) K-map & T.

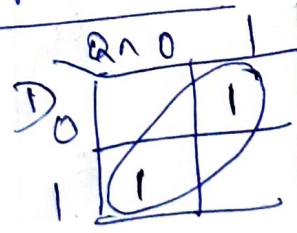

$$T = D \oplus Q_n$$

(iii)

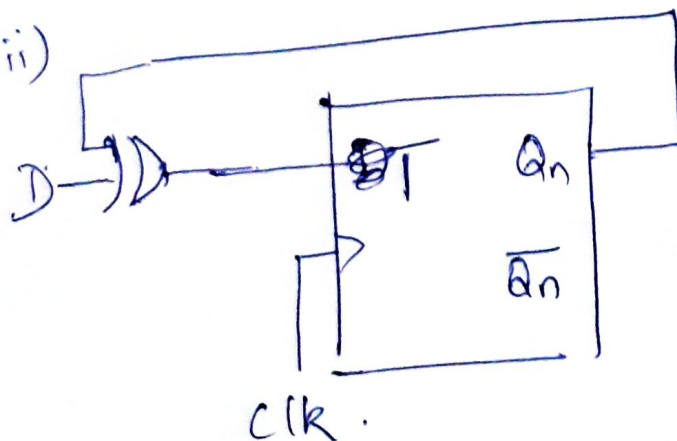

0	0	0
0	1	1
1	0	1
1	1	0

D	Qn	T
0	0	0 → 0
0	1	1 → 0
1	0	1 → 1
1	1	0 → 1

D to T flip flop conversion

T, T & T.

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

E.T & D.F.F.

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1


ii)

T	Q_n	Q_{n+1}	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

ii) K-map for D

T	Q_n	0	1
0		0	1
1		1	0

$$D = T \oplus Q_n$$

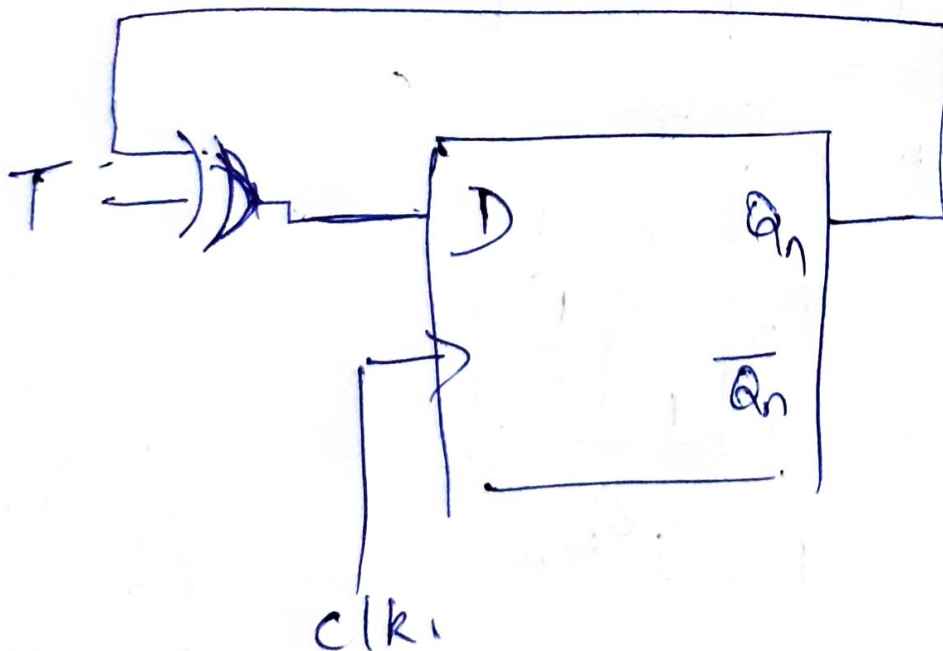

T	Q_n	D
0	0	0
0	1	1
1	0	1
1	1	0